

frequency (Hz)	input voltage V_{in} (V)	current I (mA)	V_C (V)	V_L (V)
20				
40				
60				
80				
100				
160				
200				
210				
220				
230				
240				
250				
300				
400				
500				
600				
700				
800				
900				
1000				
$f_0 =$:				

Fig 26.3

	I max mA	0.707 I max mA	f1 Hz	f2 Hz	f2 - f1 Hz
for R=1 k Ω					
for R= 0 Ω					

Fig 26.7